



Digital Design


Chapter 2: Combinational Logic Design

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>


Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites.. PowerPoint source (or pdf with animations) may **not** be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.

Introduction

 


 - Let's learn to design digital circuits
- We'll start with a simple form of circuit:
 - **Combinational circuit**
 - A digital circuit whose outputs depend solely on the present combination of the circuit inputs' values





Switches

 - Electronic switches are the basis of binary digital circuits
 - Electrical terminology
 - **Voltage**: Difference in electric potential between two points
 - Analogous to water pressure
 - **Current**: Flow of charged particles
 - Analogous to water flow
 - **Resistance**: Tendency of wire to resist current flow
 - Analogous to water pipe diameter
 - $V = I * R$ (Ohm's Law)



Switches

  - A switch has three parts
 - Source input, and output
 - Current wants to flow from source input to output
 - Control input
 - Voltage that controls whether that current can flow
- The amazing shrinking switch
 - 1930s: Relays
 - 1940s: Vacuum tubes
 - 1950s: Discrete transistor
 - 1960s: Integrated circuits (ICs)
 - Initially just a few transistors on IC
 - Then tens, hundreds, thousands...



quarter
(to see the relative size)

Brief History



- Vacuum Tubes
- 1947-Point Contact Transistor
- 1948-Bipolar Junction Transistor
- 1958-BJT based Integrated Circuit (Prototype)
- pMOSFET
- 1970s-nMOSFET
- 1980s-CMOS Technology
- 2011-FinFET



Processor	Transistor count	Date of introduction	Manufacturer	Process	Area	Processor	Transistor count	Date of introduction	Manufacturer	Process	Area
Intel 4004	2,300	1971	Intel	10 μm	12 mm ²	AMD K8	105,900,000	2003	AMD	130 nm	193 mm ²
Intel 8008	3,500	1972	Intel	10 μm	14 mm ²	Itanium 2 McKinley	220,000,000	2002	Intel	180 nm	421 mm ²
MOS Technology 6502	3,510	1975	MOS Technology	8 μm	21 mm ²	Cell	241,000,000	2006	Sony/IBM/Toshiba	90 nm	221 mm ²
Motorola 6800	4,100	1974	Motorola	6 μm	16 mm ²	Core 2 Duo	291,000,000	2006	Intel	65 nm	143 mm ²
Intel 8080	4,500	1974	Intel	6 μm	20 mm ²	Itanium 2 Madison EM	410,000,000	2003	Intel	130 nm	374 mm ²
RCA 1802	5,000	1974	RCA	5 μm	27 mm ²	AMD K10 quad-core 2M L3	463,000,000	2007	AMD	65 nm	283 mm ²
Intel 8085	6,500	1976	Intel	3 μm	20 mm ²	ARM Cortex-A9	26,000,000	2007	ARM		
Zilog Z80	8,500	1976	Zilog	4 μm	18 mm ²	AMD K10 quad-core 6M L3	758,000,000	2008	AMD	45 nm	258 mm ²
Motorola 6809	9,000	1978	Motorola	5 μm	21 mm ²	Itanium 2 with 9MB cache	592,000,000	2004	Intel	130 nm	432 mm ²
Intel 8086	29,000	1978	Intel	3 μm	33 mm ²	Core i7	731,000,000	2008	Intel	45 nm	263 mm ²
Intel 8088	29,000	1979	Intel	3 μm	33 mm ²	POWER6	789,000,000	2007	IBM	65 nm	341 mm ²
Intel 80186	55,000	1982	Intel	3 μm		6ix-Core Opteron 2400	904,000,000	2009	AMD	45 nm	346 mm ²
Motorola 68000	68,000	1979	Motorola	4 μm	44 mm ²	16-Core SPARC T3	1,000,000,000	2010	Sun/Oracle	40 nm	377 mm ²
Intel 80286	134,000	1982	Intel	1.5 μm	49 mm ²	Quad-Core + GPU Core i7	1,160,000,000	2011	Intel	32 nm	216 mm ²
Intel 80386	275,000	1985	Intel	1.5 μm	104 mm ²	6ix-Core Core i7	1,170,000,000	2010	Intel	32 nm	240 mm ²
ARM 1	25,000	1985	Acom			8-core POWER7 32ML3	1,200,000,000	2010	IBM	45 nm	567 mm ²
ARM 2	25,000	1986	Acom			8-Core AMD Bulldozer	1,200,000,000	2012	AMD	32nm	315 mm ²
Intel 80486	1,180,235	1989	Intel	1 μm	173 mm ²	Quad-Core + GPU AMD Trinity	1,303,000,000	2012	AMD	32 nm	246 mm ²
ARM 3	300,000	1989	Acom			Quad-core z196	1,400,000,000	2010	IBM	45 nm	512 mm ²
R4000	1,350,000	1991	MIPS	1.0 μm	213 mm ²	Quad-Core + GPU Core i7	1,400,000,000	2012	Intel	22 nm	160 mm ²
ARM 6	30,000	1991	ARM			Dual-Core Itanium 2	1,700,000,000	2006	Intel	90 nm	596 mm ²
Pentium	3,100,000	1993	Intel	0.8 μm	294 mm ²	6ix-Core Xeon 7400	1,900,000,000	2008	Intel	45 nm	503 mm ²
ARM 7	578977	1994	ARM		68.51 mm ²	Quad-Core Itanium Tukwila	2,000,000,000	2010	Intel	65 nm	699 mm ²
Pentium Pro	5,500,000	1995	Intel	0.5 μm	307 mm ²	8-core POWER7+ 80ML3	2,100,000,000	2012	IBM	32 nm	567 mm ²
AMD K5	4,300,000	1996	AMD	0.5 μm	251 mm ²	6ix-Core Core i716-Core Xeon E5	2,270,000,000	2011	Intel	32 nm	434 mm ²
Pentium II	7,500,000	1997	Intel	0.35 μm	195 mm ²	8-Core Xeon NehalemEX	2,300,000,000	2010	Intel	45 nm	684 mm ²
AMD K6	8,800,000	1997	AMD	0.35 μm	162 mm ²	10-Core Xeon Westmere-EX	2,600,000,000	2011	Intel	32 nm	512 mm ²
Pentium III	9,500,000	1999	Intel	0.25 μm	128 mm ²	6ix-core zEC12	2,750,000,000	2012	IBM	32 nm	597 mm ²
AMD K6-III	21,300,000	1999	AMD	0.25 μm	118 mm ²	8-Core Itanium 2	3,100,000,000	2012	Intel	32 nm	544 mm ²
AMD K7	22,000,000	1999	AMD	0.25 μm	184 mm ²	62-Core Xeon Phi	5,000,000,000	2012	Intel	22 nm	
Pentium 4	42,000,000	2000	Intel	180 nm	217 mm ²	Xbox One Main SoC	5,000,000,000	2013	Microsoft		363 mm ²
Atom	47,000,000	2008	Intel	45 nm	24 mm ²						
Barton	54,300,000	2003	AMD	130 nm	101 mm ²						

Moore's Law

- IC capacity doubling about every 18 months for several decades
 - Known as “Moore’s Law” after Gordon Moore, co-founder of Intel
 - Predicted in 1965 predicted that components per IC would double roughly every year or so
 - Book cover depicts related phenomena
 - For a particular number of transistors, the IC shrinks by half every 18 months
 - Notice how much shrinking occurs in just about 10 years
 - Enables incredibly powerful computation in incredibly tiny devices
 - Today’s ICs hold *billions* of transistors
 - The first Pentium processor (early 1990s) needed only 3 million

  


*An Intel Pentium processor IC
having millions of transistors*



The CMOS Transistor

 
- CMOS transistor
 - Basic switch in modern ICs




Silicon -- not quite a conductor or insulator:

Semiconductor

nMOS

 


conducts

 


does not conduct

pMOS

 

does not conduct

 


conducts



Boolean Logic Gates

Building Blocks for Digital Circuits


(Because Switches are Hard to Work With)

 

- “Logic gates” are better digital circuit building blocks than switches (transistors)
 - Why?...





 
Relating Boolean Algebra to Digital Design



- Implement Boolean operators using transistors
 - Call those implementations *logic gates*.



NOT/OR/AND Logic Gate Timing Diagrams

   

Boolean Algebra and its Relation to Digital Circuits

- **Boolean Algebra**

- Variables represent 0 or 1 only
- Operators return 0 or 1 only
- Basic operators
 - AND: $a \text{ AND } b$ returns 1 only when both $a=1$ and $b=1$
 - OR: $a \text{ OR } b$ returns 1 if either (or both) $a=1$ or $b=1$
 - NOT: $\text{NOT } a$ returns the opposite of a (1 if $a=0$, 0 if $a=1$)

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Evaluating Boolean Equations

- Evaluate the Boolean equation $F = (a \text{ AND } b) \text{ OR } (c \text{ AND } d)$ for the given values of variables a , b , c , and d :
 - Q1: $a=1, b=1, c=1, d=0$.

- Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 0) = 1 \text{ OR } 0 = 1$.

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0





Converting to Boolean Equations

- Convert the following English statements to a Boolean equation
 - Q1. a is 1 and b is 1.
 - Answer: $F = a \text{ AND } b$
 - Q2. either of a or b is 1.
 - Answer: $F = a \text{ OR } b$
 - Q3. both a and b are not 0.
 - Answer:
 - (a) Option 1: $F = \text{NOT}(a) \text{ AND } \text{NOT}(b)$
 - (b) Option 2: $F = a \text{ OR } b$
 - Q4. a is 1 and b is 0.
 - Answer: $F = a \text{ AND } \text{NOT}(b)$




  Example: Converting a Boolean Equation to a Circuit of Logic Gates

- Q: Convert the following equation to logic gates:
 $F = a \text{ AND NOT}(b \text{ OR NOT}(c))$



Some Circuit Drawing Conventions

 

Boolean Algebra Terminology

- Example equation: $F(a,b,c) = a'bc + abc' + ab + c$
- **Variable**
 - Represents a value (0 or 1)
 - Three variables: a, b, and c
- **Literal**
 - Appearance of a variable, in true or complemented form
 - Nine literals: a', b, c, a, b, c', a, b, and c
- **Product term**
 - Product of literals
 - Four product terms: a'bc, abc', ab, c
- **Sum-of-products**
 - Equation written as OR of product terms only
 - Above equation is in sum-of-products form. “ $F = (a+b)c + d$ ” is not.



Boolean Algebra Properties


- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
 - (this one is tricky!)
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- To prove, just evaluate all possibilities

Example uses of the properties

- Show abc' equivalent to $c'ba$.
 - Use commutative property:
 - $a*b*c' = a*c'*b = c'*a*b = c'*b*a = c'ba$.
- Show $abc + abc' = ab$.
 - Use first distributive property
 - $abc + abc' = ab(c+c')$.
 - Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
 - Identity property
 - $ab(1) = ab*1 = ab$.
- Show $x + x'z$ equivalent to $x + z$.
 - Second distributive property
 - Replace $x+x'z$ by $(x+x')*(x+z)$.
 - Complement property
 - Replace $(x+x')$ by 1,
 - Identity property
 - replace $1*(x+z)$ by $x+z$.



 Example that Applies Boolean Algebra Properties



- Found inexpensive chip that computes:
 - $f = c'hp + c'hp' + c'h'p$
 - Can we use it?
 - Is it the same as $f = c'(p+h)$?
- Use Boolean algebra:

$$f = c'hp + c'hp' + c'h'p$$

$$f = c'h(p + p') + c'h'p \quad (\text{by the distributive property})$$

$$f = c'h(1) + c'h'p \quad (\text{by the complement property})$$

$$f = c'h + c'h'p \quad (\text{by the identity property})$$

$$f = hc' + h'pc' \quad (\text{by the commutative property})$$

Same!



Boolean Algebra: Additional Properties

- Null elements

- $a + 1 = 1$
- $a * 0 = 0$

- Idempotent Law

- $a + a = a$
- $a * a = a$

- Involution Law

- $(a')' = a$

- DeMorgan's Law

- $(a + b)' = a'b'$
- $(ab)' = a' + b'$
- Very useful!

- To prove, just evaluate all possibilities

Aircraft lavatory sign example



- Equation and circuit

- $S = a' + b' + c'$


- Transform

- $(abc)' = a' + b' + c'$ (by DeMorgan's Law)
 - $S = (abc)'$

- New equation and circuit

  

Representations of Boolean Functions

 

- A function can be represented in different ways
 - Above shows seven representations of the same functions $F(a,b)$, using four different methods: English, Equation, Circuit, and Truth Table



Truth Table Representation of Boolean Functions

- Define value of F for each possible combination of input values
 - 2-input function: 4 rows
 - 3-input function: 8 rows
 - 4-input function: 16 rows
- Q: Use truth table to define function $F(a,b,c)$ that is 1 when abc is 5 or greater in binary

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

a

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(c)



Converting among Representations

- Can convert from any representation to any other
- Common conversions
 - Equation to circuit
 - Truth table to equation
 - Equation to truth table
 - Easy -- just evaluate equation for each input combination (row)
 - Creating intermediate columns helps

Inputs		Outputs	Term
a	b	F	F = sum of
0	0	1	a'b'
0	1	1	a'b
1	0	0	
1	1	0	

$$F = a'b' + a'b$$

Q: Convert to equation

a	b	c	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	ab'c
1	1	0	1	abc'
1	1	1	1	abc

$$F = ab'c + abc' + abc$$

Q: Convert to truth table: $F = a'b' + a'b$

Inputs				Output
a	b	a'b'	a'b	F
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0



Standard Representation: Truth Table

- How can we determine if two functions are the same?
 - Use algebraic methods
 - But if we failed, does that prove *not* equal? No.
- Solution: Convert to truth tables
 - Only ONE truth table representation of a given function
 - **Standard** representation -- for given function, only one version in standard form exists

$$f = c'h p + c'h p' + c'h'$$

$$f = c'h(p + p') + c'h'p$$

$$f = c'h(1) + c'h'p$$

$$f = c'h + c'h'p$$

(what if we stopped here?)

$$f = hc' + h'pc'$$

F = ab + 'a			F = a'b' + a'b + ab		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	1	1	1	1	1

Same



Canonical Form -- Sum of Minterms

- Truth tables too big for numerous inputs
- Use standard form of equation instead
 - Known as **canonical form**
 - Regular algebra: group terms of polynomial by power
 - $ax^2 + bx + c$ ($3x^2 + 4x + 2x^2 + 3 + 1 \rightarrow 5x^2 + 4x + 4$)
 - Boolean algebra: create sum of minterms
 - **Minterm**: product term with every function literal appearing exactly once, in true or complemented form
 - Just multiply-out equation until sum of product terms
 - Then expand each term until all terms are minterms

Q: Determine if $F(a,b)=ab+a'$ is same function as $F(a,b)=a'b'+a'b+ab$, by converting first equation to canonical form (second already in canonical form)

$F = ab+a'$ (already sum of products)


$F = ab + a'(b+b')$ (expanding term)

$F = ab + a'b + a'b'$ (SAME -- same three terms as other equation)




Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex: $F = \underline{ab} + c'$, $G = \underline{ab} + bc$

 

Option 1: Separate circuits

 


Option 2: Shared gates



Multiple-Output Example: BCD to 7-Segment Converter

TABLE 2-4 4-bit binary number to seven-segment display truth table

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

abcdefg =

(a)



1111110



0110000



1101101

(b)

$$a = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

$$b = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz + wx'y'z' + wx'y'z$$




Combinational Logic Design Process

Step	Description
Step 1 Capture the function	Create a truth table or equations, <i>whichever is most natural for the given problem</i> , to describe the desired behavior of the combinational logic.
Step 2 Convert to equations	This step is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.
Step 3 Implement as a gate-based circuit	For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)




Example: Three 1s Detector

 
- Problem: Detect three consecutive 1s in 8-bit input: abcdefgh
 - 000**111**01 → 1 10101011 → 0
 - **111**10000 → 1
- **Step 1: Capture** the function
 - Truth table or equation?
 - Truth table too big: $2^8=256$ rows
 - Equation: create terms for each possible case of three consecutive 1s
 - $y = abc + bcd + cde + def + efg + fgh$
- **Step 2: Convert** to equation -- already done
- **Step 3: Implement** as a gate-based circuit




More Gates

 


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

 



x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

 

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

 

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1


 
 


- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: Exactly 1 input is 1, for 2-input XOR. (For more inputs -- odd number of 1s)
- XNOR: Opposite of XOR (“NOT XOR”)
- NAND same as AND with power & ground switched
 - Why? nMOS conducts 0s well, but not 1s (reasons beyond our scope) -- so NAND more efficient
- Likewise, NOR same as OR with power/ground switched
- AND in CMOS: NAND with NOT
- OR in CMOS: NOR with NOT
- So NAND/NOR more common




More Gates: Example Uses

   - Aircraft lavatory sign example
 - $S = (abc)'$
- Detecting all 0s
 - Use NOR
- Detecting equality
 - Use XNOR
- Detecting odd # of 1s
 - Use XOR
 - Useful for generating “parity” bit common for detecting errors







Completeness of NAND

 - Any Boolean function can be implemented *using just NAND gates*. Why?
 - Need AND, OR, and NOT
 - NOT: 1-input NAND (or 2-input NAND with inputs tied together)
 - AND: NAND followed by NOT
 - OR: NAND preceded by NOTs
- Likewise for NOR




Decoders and Muxes

- **Decoder:** Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
 - So has four outputs, one for each possible input binary number
- Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if $e=0$
 - Regular behavior if $e=1$
- n -input decoder: 2^n outputs

    


Multiplexor (Mux)




 
- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux $\rightarrow$ needs 2 select inputs to indicate which input to route through
 - 8 input mux $\rightarrow$ 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects
 - Like a railyard switch




Mux Internal Design

 

2x1 mux

    


4x1 mux

 


Mux Example

 - City mayor can set four switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux




Muxes Commonly Together -- N-bit Mux

 

- Ex: Two 4-bit inputs, A (a3 a2 a1 a0), and B (b3 b2 b1 b0)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B



N-bit Mux Example


 


- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide
 - Choose which to display using two inputs x and y
 - Use 8-bit 4x1 mux



Additional Considerations

Non-Ideal Gate Behavior -- Delay

  

- Real gates have some delay
 - Outputs don't change immediately after inputs change



Chapter Summary

- Combinational circuits
 - Circuit whose outputs are function of present inputs
 - No “state”
- Switches: Basic component in digital circuits
- Boolean logic gates: AND, OR, NOT -- Better building block than switches
 - Enables use of Boolean algebra to design circuits
- Boolean algebra: uses true/false variables/operators
- Representations of Boolean functions: Can translate among
- Combinational design process: Translate from equation (or table) to circuit through well-defined steps
- More gates: NAND, NOR, XOR, XNOR also useful
- Muxes and decoders: Additional useful combinational building blocks

